

Ex1: (05 points)

(1)

1. $i_g = 0 \quad (V_A - V_B = 0)$

$$V_A - V_B = (V_A - V_C) + (V_C - V_B) = -R_1 i_1 + R_2 i_2 \Rightarrow R_1 i_1 = R_2 i_2$$

$$= R_4 i_1 \neq R_3 i_2 = 0 \Rightarrow R_4 i_1 = R_3 i_2 \Rightarrow i_1 = \frac{R_3 i_2}{R_4}$$

$$R_1 \cdot \frac{R_3}{R_4} i_2 = R_2 i_2 \Rightarrow \boxed{R_1 R_3 = R_2 R_4} \quad (2)$$

2. Pont équilibré \Rightarrow ajuster un courant.

(1)

3. $C = 0$

$$\begin{aligned} E_{th} &= (V_A - V_B)_o = -R_1 i_1 + R_2 i_2 & i_2 = i_3 = \frac{e}{R_2 + R_3} \\ &= R_4 i_2 + R_3 i_1 & i_1 = i_4 = \frac{e}{R_1 + R_4} \end{aligned}$$

$$\begin{aligned} E_{th} &= -R_1 \cdot \frac{e}{R_1 + R_4} + R_2 \cdot \frac{e}{R_2 + R_3} = e \left(\frac{R_2(R_1 + R_4) - R_1(R_2 + R_3)}{(R_1 + R_4)(R_2 + R_3)} \right) \\ &= \frac{-10}{5} + \frac{2 \times 10}{5} = -2 + 4 = 2 \text{ V.} \end{aligned}$$

$$R_{th} = R_1 \parallel R_4 + R_2 \parallel R_3 = \frac{1 \cdot 4}{1+4} + \frac{2 \cdot 3}{2+3} = \frac{4}{5} + \frac{6}{5} = \frac{10}{5} = 2 \Omega$$

$$i_g = \frac{E_{th}}{R_{th} + g} = \frac{2}{2+2} = 0,5 \text{ A} \quad (2)$$

Ex 2: 05 pts

(2)

$$1 - i = C \frac{dV_s}{dt} \quad (0,5)$$


$$2 - V_e = Ri + V_s \quad (0,5)$$

$$3 - V_e = V_s + C \frac{dV_s}{dt} \quad (0,5)$$

$$4 - V_e = E \quad t > 0 \quad V_s(t) = \lambda e^{-\frac{t}{C}} + E$$

$$\text{à } t=0 \quad V_s(0) = 0 \Rightarrow E = -\lambda$$
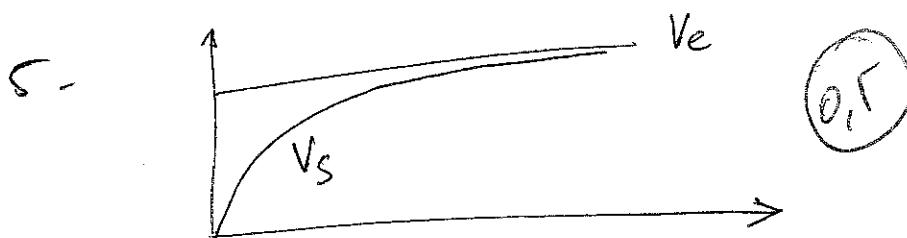
$$V_s(t) = E \left(1 - e^{-\frac{t}{C}} \right) \quad (1)$$



$$6 - V_e(t) = at \quad t > 0$$


on réinjecte l'équation proposée

$$at = at + \beta + \gamma \exp(-\frac{t}{C}) + \zeta \left[\alpha - \frac{\gamma}{C} \exp(-\frac{t}{C}) \right] \quad (1)$$

$$at = at + \beta + \alpha \zeta$$

D'où par identification $\alpha = \alpha$ et $\beta = -\alpha \zeta = -\alpha C$
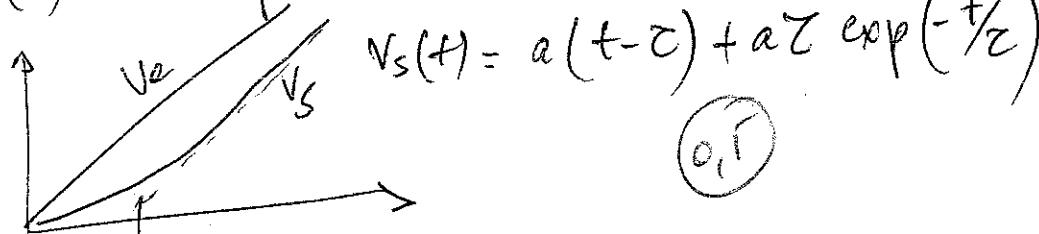
$$\text{à } t=0 \quad V_s(0) = 0 \Rightarrow \beta = -\gamma \Rightarrow \gamma = \alpha C$$



$$8 - t \gg C \Rightarrow \exp(-\frac{t}{C}) \rightarrow 0 \Rightarrow V_s = \alpha(t - C)$$

D'où décalage de C de V_s / V_e .

(0,5)

Ex3: 25 pts

(3)

$$1 - E_{th} = \frac{Z_R \cdot e(f)}{Z_R + Z_L} = \frac{R e(f)}{R + \frac{1}{j \omega}} = \frac{j e(f)}{1+j}$$

$$E_{th} = \frac{E_0 e^{j(\omega t + \pi/2)}}{\sqrt{2} \exp j\pi/4} = \frac{E_0}{\sqrt{2}} e^{j(\omega t + \pi/4)} \quad (1)$$

$$Z_{th} = \frac{1}{j \omega} + \frac{R}{1+j R \omega} = \frac{R}{j R \omega} + \frac{R}{1+j R \omega} = \frac{R}{j} + \frac{R}{1+j}$$

$$Z_{th} = R \left(-j + \frac{1}{1+j} \right) = R \left(-j + \frac{1-j}{2} \right) = \frac{R}{2} \left(1 - 3j \right)$$

$$a = \frac{R}{2}, \quad b = -\frac{3R}{2}$$

$$|Z_{th}| = \sqrt{\left(\frac{R}{2}\right)^2 + \left(\frac{-3R}{2}\right)^2} = \frac{R}{2} \sqrt{1+9} = \frac{R\sqrt{10}}{2} \quad (1)$$

$$\varphi = \arctan \left(\frac{-3}{1} \right) = -\arctan 3$$

$$2 - \eta = \frac{E_{th}}{Z_{th}} = \frac{\frac{E_0}{\sqrt{2}} e^{j(\omega t + \pi/4)}}{\frac{R\sqrt{10}}{2} e^{+j\varphi}} = \frac{2E_0}{R\sqrt{20}} e^{j(\omega t + \pi/4 - \varphi)} \quad (1)$$

$$\eta = \frac{E_0}{R\sqrt{2}} \exp j(\omega t + \pi/4 - \varphi)$$

$$3 - i_R = \frac{E_{th}}{Z_{th} + R} = \frac{E_{th}}{\frac{R}{2}(1-3j) + R} = \frac{E_{th}}{\frac{R}{2}(1-3j+2)} = \frac{E_{th}}{\frac{2E_0}{R\sqrt{20}}} = \frac{E_{th}}{\frac{R}{2}(3-3j)} \quad (1)$$

$$i_R = \frac{2E_{th}}{3R(1-j)} = \frac{2E_{th}}{3R\sqrt{2}} e^{-j\pi/4} = \frac{2E_0}{3R\sqrt{2}\sqrt{2}} e^{-j(\omega t + \pi/4 + \pi/4)}$$

$$i_R = \frac{E_0}{3R} e^{j(\omega t + \pi/2)} \quad (1)$$

Ex4: 05 pts

(4)

$$1 - Z_{RL} = R + jL\omega \quad (1)$$

$$2 - Z_{RC} = R + \frac{1}{jC\omega} \quad (1)$$

$$3 - Z_T = Z_{RL} \parallel Z_{RC} = \frac{(R + jL\omega)(R + \frac{1}{jC\omega})}{(R + jL\omega) + (R + \frac{1}{jC\omega})} = \frac{R^2 + jL\omega R + \frac{R}{jC\omega} + \frac{L}{C}}{2R + j(L\omega - \frac{1}{C\omega})}$$

$$Z_T = \frac{(R^2 + \frac{L}{C}) + jR(L\omega - \frac{1}{C\omega})}{2R + jB} \quad A = R^2 + \frac{L}{C}$$

$$\textcircled{2} \quad B = L\omega - \frac{1}{C\omega}$$

$$\text{Si } LC\omega^2 = 1 \Rightarrow B = 0$$

$$Z_T = \frac{R^2 + \cancel{jC}}{2R} \quad LC\omega^2 = 1 \Rightarrow LC = \frac{1}{\omega^2}$$

$$Z_T = \frac{R^2 + L^2\omega^2}{2R} = \frac{R}{2} + \frac{L^2\omega^2}{2R} \quad C = \frac{1}{LC\omega^2} \quad \frac{LC}{C^2} = \frac{1}{\omega^2 C^2}$$

$$\textcircled{1}$$