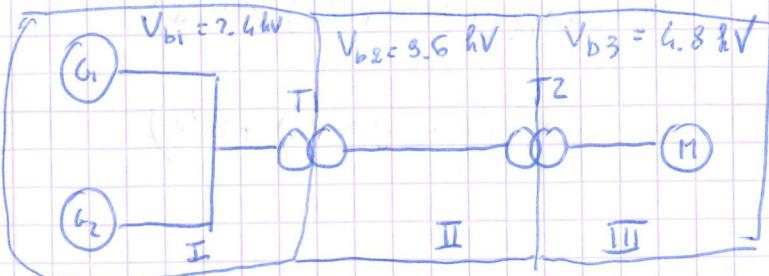


- ER51 - 25 June 2024

- Exercise 1 -

$$S_b = 100 \text{ kVA} = 0.1 \text{ MVA} \quad V_b = 2400 \text{ V} = 2.4 \text{ kV} \quad (\text{in section I where the generators are})$$



$$Z_{\text{new}} = Z_{\text{old}} \left( \frac{S_{\text{new}}}{S_{\text{old}}} \right) \left( \frac{V_{\text{old}}}{V_{\text{new}}} \right)^2$$

$$\begin{aligned} G_1 & 10 \text{ kVA} \\ & 2.4 \text{ kV} \\ z &= j0.2 \end{aligned}$$

$$Z_{G_1} = j0.2 \left( \frac{100}{10} \right) \left( \frac{2.4}{2.4} \right)^2 = j2 \text{ pu}$$

$$\begin{aligned} G_2 & 20 \text{ kVA} \\ & 2.4 \text{ kV} \\ z &= j0.2 \end{aligned}$$

$$Z_{G_2} = j0.2 \left( \frac{100}{20} \right) \left( \frac{2.4}{2.4} \right)^2 = j1 \text{ pu}$$

$$\begin{aligned} T_1 & 40 \text{ kVA} \\ & 2.4 / 3.6 \\ z &= j0.1 \end{aligned}$$

$$Z_{T_1} = j0.1 \left( \frac{100}{40} \right) \left( \frac{2.4}{2.4} \right)^2 = 0.25$$

$$\text{In zone III we have } \frac{V_{b2}}{V_{b3}} = \frac{10}{5} \Rightarrow V_{b3} = \frac{5}{10} V_{b2} = \frac{3.6}{2.4} = 1.5 \text{ kV}$$

$$\begin{aligned} T_2 & 80 \text{ kVA} \\ & 10 / 5 \text{ kV} \\ z &= j0.1 \end{aligned}$$

$$Z_{T_2} = j0.1 \left( \frac{100}{80} \right) \left( \frac{10}{3.6} \right)^2 = j0.136 \text{ pu}$$


$$\text{In zone II the line impedance is } Z_{b2} = \frac{V_{b2}}{S_b} = \frac{(3.600)}{100 \cdot 10^3} = 36 \text{ ohms}$$

The line is  $z = 50 + j200 \text{ ohms}$  in pu

$$Z = \frac{z}{Z_{b2}} = \frac{50 + j200}{36} = 0.054 + j0.217 \text{ pu}$$

$$\text{M: } 25 \text{ kVA} \quad \text{Thus in pu, } S_M = \frac{25 \text{ kVA}}{100} = 0.25$$
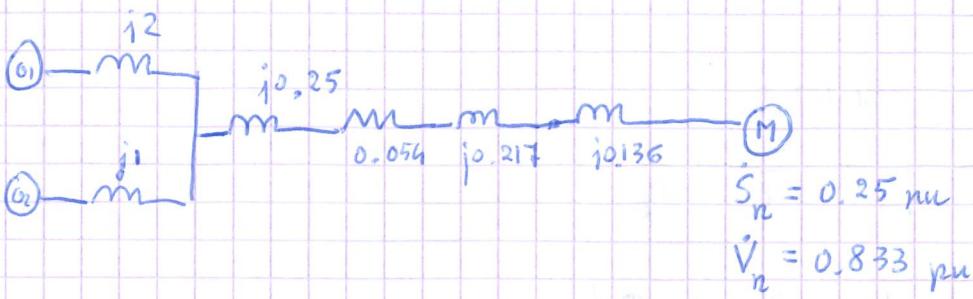
$$V_n = \frac{4}{4.8} = 0.833 \text{ pu}$$



## - Exercise 2 -

This exercise is explained in lecture 1, slide 31.

We have

$$L_1 = \frac{\mu_0}{2\pi} \left( \frac{1}{4} + \ln \frac{1}{R_1} \right) - \frac{\mu_0}{2\pi} \ln \frac{1}{D}$$

$$L_2 = \frac{\mu_0}{2\pi} \left( \frac{1}{4} + \ln \frac{1}{R_2} \right) - \frac{\mu_0}{2\pi} \ln \frac{1}{D}$$

Total inductance is therefore:

$$L = L_1 + L_2 = \frac{\mu_0}{2\pi} \left( \frac{2}{4} + \ln \frac{1}{R_1} + \ln \frac{1}{R_2} \right) - \frac{\mu_0}{2\pi} \ln \frac{1}{D} = \frac{\mu_0}{2\pi} \ln \frac{1}{D}$$

$$= \frac{\mu_0}{8\pi} \left( \frac{1}{2} + \ln \frac{1}{R_1 R_2} \right) - \frac{\mu_0}{2\pi} \ln \frac{1}{D} =$$

$$= \cancel{\frac{\mu_0}{2\pi} \ln \frac{1}{VR_1 R_2}} = \frac{\mu_0}{\pi} \left( \frac{1}{4} + \frac{1}{2} \ln \frac{1}{R_1 R_2} \right) - \frac{\mu_0}{2\pi} \ln \frac{1}{D} =$$

$$= \frac{\mu_0}{\pi} \left( \frac{1}{4} + \ln \frac{1}{\sqrt{R_1 R_2}} - \ln \frac{1}{D} \right) =$$

$$= \frac{\mu_0}{\pi} \left( \frac{1}{4} + \ln \frac{D}{\sqrt{R_1 R_2}} \right) \text{ H/m.}$$

Ex m. 3

On  $P_1$  on the surface of conductor 1

$$V_{P_1} = \frac{Q}{2\pi\epsilon_0} \ln \frac{1}{R_1} - \frac{Q}{2\pi\epsilon_0} \ln \frac{1}{D}$$

$$V_{P_2} = -\frac{Q}{2\pi\epsilon_0} \ln \frac{1}{R_2} + \frac{Q}{2\pi\epsilon_0} \ln \frac{1}{D}$$

$$\Delta V = V_{P_1} - V_{P_2} = \frac{Q}{2\pi\epsilon_0} \left( \ln \frac{1}{R_1} - \ln \frac{1}{D} + \ln \frac{1}{R_2} - \ln \frac{1}{D} \right) =$$

$$\ln \frac{1}{D} = -\ln D = \frac{Q}{2\pi\epsilon_0} \left( \ln D^2 + \ln \frac{1}{R_1 R_2} \right) = \frac{Q}{\pi\epsilon_0} \left( \frac{i}{2} \ln \frac{D^2}{R_1 R_2} \right) =$$
$$= \frac{Q}{\pi\epsilon_0} \ln \frac{D}{\sqrt{R_1 R_2}}$$

Thus  $C = \frac{Q}{\Delta V} = \frac{\pi\epsilon_0}{\ln \frac{D}{\sqrt{R_1 R_2}}}$

Since  $R_1 = R_2 = R$

$$C = \frac{\pi\epsilon_0}{\ln \frac{D}{R}}$$

- E.m. 4 -

c) ~~assume~~ The line is not lossless (only  $\alpha = 0$ ) and is long ( $\approx 300 \text{ km}$ )

$$Z_w = \sqrt{\frac{Z_b}{Y_p}} = \sqrt{\frac{R+j\omega L}{G+j\omega C}} = \sqrt{\frac{0.03 + j0.4}{j5 \cdot 10^{-6}}} = 283 \cdot 2 \angle -2.14^\circ$$

$$= 283 \cdot 10^2 - j106 \cdot 10 =$$

the line is slightly capacitive as expected.

$$= 283 - j10.6$$

$$\gamma = \sqrt{(R+j\omega L)(G+j\omega C)} = 0.0001 + j0.0014 =$$

$$= 0.001416 \angle 87.85^\circ \text{ km}^{-1}$$

b)

$$\begin{bmatrix} V(0) \\ I(0) \end{bmatrix}^T = \begin{bmatrix} \text{Ch} \gamma l & Z_w \text{Sh} \gamma l \\ \frac{1}{Z_w} \text{Sh} \gamma l & \text{Ch} \gamma l \end{bmatrix} \cdot \begin{bmatrix} V(l) \\ I(l) \end{bmatrix}$$

$$\gamma l = \gamma l = 0.0153 + j0.426 = 0.4263 \angle 87.85^\circ$$

$$\text{Ch} \gamma l = 0.3113 + j0.0065 = 0.3114 \angle 0.411^\circ$$

$$\text{Sh} \gamma l = 0.0165 + j0.4120 = 0.4122 \angle 87.98^\circ$$

$$Z_w \text{Sh} \gamma l = 8.672 + j1.1645 \cdot 10^2 = 116.76 \angle 85.84^\circ$$

$$\frac{1}{Z_w} \text{Sh} \gamma l = -0 + j0.0015 \Rightarrow \cancel{0.0015} \angle 90^\circ$$

$-10^{-4}$ . This explains the angle slightly higher than  $90^\circ$

~~T~~

$$\begin{bmatrix} V(l) \\ I(l) \end{bmatrix} = \begin{bmatrix} 345 \\ 0 \end{bmatrix} \Rightarrow \begin{bmatrix} V(0) \\ I(0) \end{bmatrix} = T \begin{bmatrix} 345 \\ 0 \end{bmatrix}$$

Thus

$$\begin{bmatrix} V(0) \\ I(0) \end{bmatrix} = \begin{bmatrix} 314.41 + j2.26 \\ j0.5 \end{bmatrix} \Rightarrow |V(0)| = 314.42 \text{ kV}$$

c)  $Z_b = Z_w \text{Sh} \gamma l = 8.67 + j11.45$

$$Y_p = \frac{1}{Z_b} Y_p = \left( \frac{1}{Z_b} T_h \left( \frac{\gamma l}{2} \right) \right) \approx j7.616 \cdot 10^{-4}$$

