

ER57

18 gennaio 2024

Let's define

$$\delta = \delta_1 - \delta_2$$

~~Thus if the current I_2 is lagging V_1~~

we have then

$$I_{12} = \frac{V_1 - V_2}{jX}$$

Then

$$\begin{aligned}
 P_2 + jQ_2 &= V_2 I_2^* = V_2 \left(\frac{V_1 - V_2}{jX} \right)^* = \frac{V_2 V_1^* - V_2 V_2^*}{-jX} = \\
 &= \frac{V_2 V_1^* - V_2 V_2^*}{-jX} = \frac{|V_2| e^{j\delta_2} |V_1| e^{-j\delta_1} - |V_2| e^{j\delta_2} |V_2| e^{-j\delta_2}}{-jX} = \\
 &= \frac{|V_1| |V_2| e^{-j\delta} - |V_2|^2}{-jX} = \left(-\frac{1}{j} = j \right) = \\
 &= \frac{j |V_1| |V_2| e^{-j\delta} - j |V_2|^2}{X} = \frac{j |V_1| |V_2| [\cos\delta - j\sin\delta] - j |V_2|^2}{X} = \\
 &= \frac{|V_1| |V_2| \sin\delta + j (|V_1| |V_2| \cos\delta - |V_2|^2)}{X} = \\
 &= \frac{|V_1| |V_2| \sin\delta}{X} + j \left(\frac{|V_1| |V_2| \cos\delta - |V_2|^2}{X} \right)
 \end{aligned}$$

3) Thus $P_2 = \frac{|V_1| |V_2| \sin\delta}{X}$


4) $Q_2 = \frac{|V_1| |V_2| \cos\delta - |V_2|^2}{X}$

1) Since there is no ^{real} loss in the line $P_1 = P_2 = \frac{|V_1| |V_2| \sin\delta}{X}$

2-) Q_1 is easily found considering $S_1 = P_1 + jQ_1 = V_1 I_1^* = V_1 \left(\frac{V_1 - V_2}{jX} \right)^* =$

$$\begin{aligned}
 \delta = \delta_1 - \delta_2 &= \frac{V_1 V_1^* - V_1 V_2^*}{-jX} = \frac{|V_1|^2 - |V_1| |V_2| e^{j\delta}}{-jX} = \frac{-j |V_1|^2 - j |V_1| |V_2| (\cos\delta + j\sin\delta)}{X} = \\
 &= \frac{|V_1| |V_2| \sin\delta}{X} + j \frac{|V_1|^2 - |V_1| |V_2| \cos\delta}{X} \Rightarrow Q_1 = \frac{|V_1|^2 - |V_1| |V_2| \cos\delta}{X}
 \end{aligned}$$

Question 2

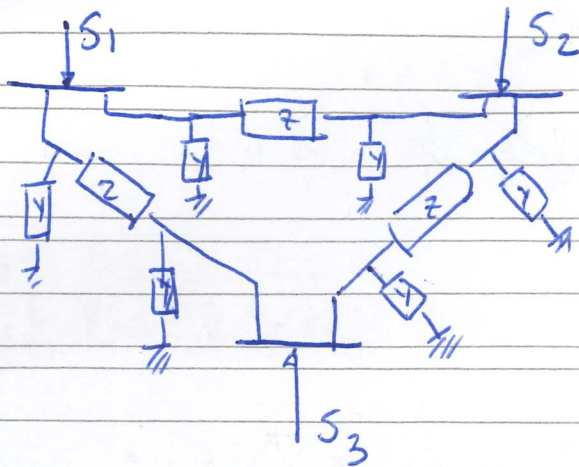

$$Y_{BUS} = \begin{bmatrix} 2Y + \frac{2}{Z} & -\frac{1}{Z} & -\frac{1}{Z} \\ -\frac{1}{Z} & 2Y + \frac{2}{Z} & -\frac{1}{Z} \\ -\frac{1}{Z} & -\frac{1}{Z} & 2Y + \frac{2}{Z} \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} & y_{13} \\ y_{21} & y_{22} & y_{23} \\ y_{31} & y_{32} & y_{33} \end{bmatrix}$$

We know that

$$I_1 = \frac{S_1^*}{V_1^*} = y_{11} V_1 + y_{12} V_2 + y_{13} V_3$$

$$I_2 = \frac{S_2^*}{V_2^*} = y_{21} V_1 + y_{22} V_2 + y_{23} V_3$$

$$I_3 = \frac{S_3^*}{V_3^*} = y_{31} V_1 + y_{32} V_2 + y_{33} V_3$$

i) But

$$S_1^* = P_1 - jQ_1 = y_{11} V_1 V_1^* + y_{12} V_1^* V_2 + y_{13} V_1^* V_3 = V_1^* \sum_{k=1}^3 y_{1k} V_k$$

$$S_2^* = P_2 - jQ_2 = y_{21} V_1 V_2^* + y_{22} V_2 V_2^* + y_{23} V_3 V_2^* = V_2^* \sum_{k=1}^3 y_{2k} V_k$$

$$S_3^* = P_3 - jQ_3 = y_{31} V_1 V_3^* + y_{32} V_2 V_3^* + y_{33} V_3 V_3^* = V_3^* \sum_{k=1}^3 y_{3k} V_k$$

These are the LFE in complex form

2) since $V_i = |V_i| e^{j\delta_i}$ ($i=1, 2, 3$)

$y_{ij} = |y_{ij}| \angle \gamma_{ij}$ we have

$$P_i - jQ_i = \sum_{k=1}^3 |y_{ik}| |V_i| |V_k| e^{j(\delta_k - \delta_i + \gamma_{ik})} \quad i=1, 2, 3.$$

Thus

$$P_1 = P_{G1} - P_{D1} = |y_{11}| |V_1| |V_1| \cos(\gamma_{11}) + |y_{12}| |V_1| |V_2| \cos(\delta_2 - \delta_1 + \gamma_{12}) + |y_{13}| |V_1| |V_3| \cos(\delta_3 - \delta_1 + \gamma_{13})$$

$$P_2 = P_{G2} - P_{D2} = |y_{21}| |V_2| |V_1| \cos(\delta_1 - \delta_2 + \gamma_{21}) + |y_{22}| |V_2|^2 \cos(\gamma_{22}) + |y_{23}| |V_2| |V_3| \cos(\delta_3 - \delta_2 + \gamma_{23})$$

$$P_3 = P_{G3} - P_{D3} = |y_{31}| |V_3| |V_1| \cos(\delta_1 - \delta_3 + \gamma_{31}) + |y_{32}| |V_3| |V_2| \cos(\delta_2 - \delta_3 + \gamma_{32}) + |y_{33}| |V_3|^2 \cos(\gamma_{33})$$

And

$$-Q_1 = Q_{G1} - Q_{D1} = |y_{11}| |V_1|^2 \sin(\gamma_{11}) + |y_{12}| |V_1| |V_2| \sin(\delta_2 - \delta_1 + \gamma_{12}) + |y_{13}| |V_1| |V_3| \sin(\delta_3 - \delta_1 + \gamma_{13})$$

$$-Q_2 = Q_{G2} - Q_{D2} = |y_{21}| |V_1| |V_2| \sin(\delta_1 - \delta_2 + \gamma_{21}) + |y_{22}| |V_2|^2 \sin(\gamma_{22}) + |y_{23}| |V_2| |V_3| \sin(\delta_3 - \delta_2 + \gamma_{23})$$

$$-Q_3 = Q_{G3} - Q_{D3} = |y_{31}| |V_3| |V_1| \sin(\delta_1 - \delta_3 + \gamma_{31}) + |y_{32}| |V_3| |V_2| \sin(\delta_2 - \delta_3 + \gamma_{32}) + |y_{33}| |V_3|^2 \sin(\gamma_{33})$$

Question 3

1) load on G1 = x MW

load on G2 = $300 - x$ MW

Reduction in frequency Δf

$$\Delta f = -R_1 \Delta P_{g1} = -\frac{0.04 \cdot 50}{100} x$$

$$\Delta f = -R_2 \Delta P_{g2} = -\frac{0.05 \cdot 50}{300} (300 - x)$$

Since the frequency is the same at steady-state, we have

$$-R_1 \Delta P_{g1} = -R_2 \Delta P_{g2} \Rightarrow$$

$$\frac{0.04 \cdot 50}{100} x = \frac{0.05 \cdot 50}{300} (300 - x)$$

$$0.02 x = 0.0083 (300 - x)$$

$$x = 88.34$$

$$300 - x = 211.6$$

Thus generator 1 will supply 88.34 MW

" 2 " " 211.6 MW

2) The system frequency is therefore

$$f = 50 - 0.02 \cdot 88.34 = 48.23 \text{ Hz}$$

Q 4

The two ~~generators~~ ^{should} pick up 20 MW and 200 MW.

$$\left(\frac{60}{600} = \frac{1}{10} \quad \text{so} \quad \frac{20}{200} = \frac{1}{10} \right) \quad \text{or} \quad \dots$$

x = load of generator 1

y = load of generator 2

Since we want the two generators to share the load in the same ratio of the nominal power ($60/600 = \frac{1}{10}$), then we must have:

$$\begin{cases} \frac{x}{y} = \frac{1}{10} \\ x + y = 220 \end{cases} \quad \rightarrow \quad x = 20 \quad y = 200$$

From the formula $\Delta P_T = -\frac{1}{R} \Delta f$ we have

$$R_1 = - \frac{\Delta f}{\Delta P_{T1}} = - \frac{-0.5}{20} = 0.025 \text{ Hz/MW}$$

$$R_2 = - \frac{\Delta f}{\Delta P_{T2}} = - \frac{-0.5}{200} = 0.0025 \text{ Hz/MW}$$

If we express R in $\mu\text{Hz}/\mu\text{MW}$ we have


$$1) \quad R_1 = 0.025 \frac{60}{50} = 0.03 \mu\text{Hz}/\mu\text{MW}$$

$$R_2 = 0.0025 \frac{600}{50} = 0.03 \mu\text{Hz}/\mu\text{MW}$$

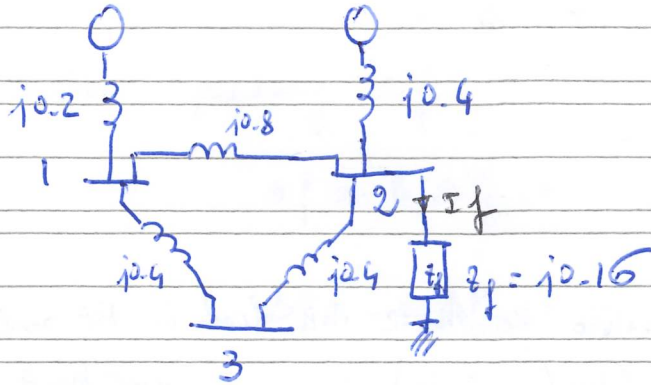2) Generators working in parallel on the same network ought to have the same regulation expressed in $\mu\text{Hz}/\mu\text{MW}$ of their own rating, in order to share load changes in proportion to their own ratings.

Ex. 5


The ~~the~~ situation is depicted in fig below




$$V_2(0) = 1 \mu u$$

$$V_1(0) = V_2(0) = V_3(0) = 1 \mu u$$

The Thevenin's equivalent circuit is

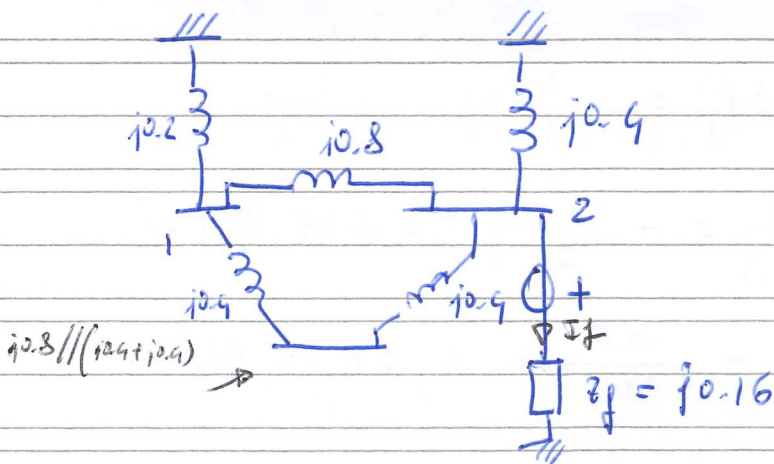

This becomes

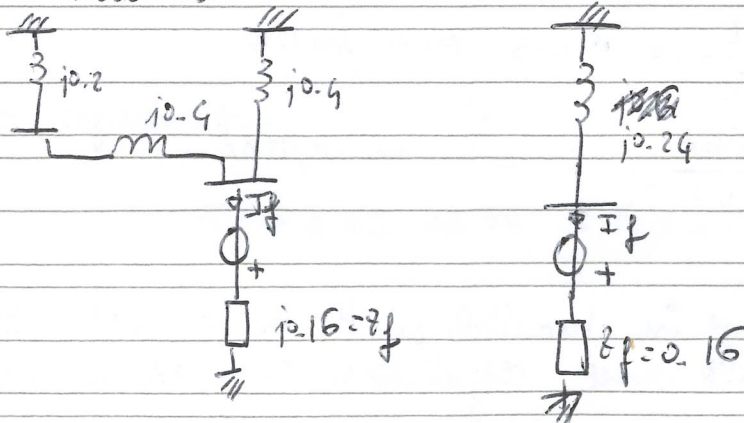

$$Z_{th} = (j0.4) // (j0.2 + j0.4) = j0.24$$

$$I_f = \frac{V_2(0)}{Z_{th} + Z_f} = \frac{1}{j0.24 + j0.16} = -j 2.5 \mu u$$

Thus $I_{G1} = \frac{j0.4}{j0.4 + j0.6} I_f = \frac{j0.4}{j0.4 + j0.6} (-j2.5) = -j \mu$

$$I_{G2} = \frac{j0.6}{j0.4 + j0.6} (-j2.5) = -j1.5$$

2) The bus voltages changes are

$$\Delta V_1 = - (j0.2)(-j) = -0.2 \mu$$

$$\Delta V_2 = - (j0.4)(-j1.5) = -0.6 \mu$$

$$\Delta V_3 = \Delta V_1 + \frac{I_{G1}}{2} j0.4 = -0.2 - (j0.4)\left(\frac{-j}{2}\right) = -0.4 \mu$$

Thus the bus voltages are

$$V_1 = V_1 + \Delta V_1 = 1 - 0.2 = 0.8 \mu$$

$$V_2 = V_2 + \Delta V_2 = 1 - 0.6 = 0.4 \mu$$

$$V_3 = V_3 + \Delta V_3 = 1 - 0.4 = 0.6 \mu$$

3) The short-circuit currents in the lines are :

$$I_{12} = \frac{V_1 - V_2}{Z_{12}} = \frac{0.8 - 0.4}{j0.8} = -j0.5 \mu$$

$$I_{13} = \frac{V_1 - V_3}{Z_{13}} = \frac{0.8 - 0.6}{j0.4} = -j0.5 \mu$$

$$I_{32} = I_{13} = \frac{0.6 - 0.4}{j0.4} = -j0.5 \mu$$

obviously all three line currents are the same