

SOLUTION QUESTION 1

The base impedance for line is

$$Z_B = \frac{(400)^2}{100} = 1,600\Omega$$

and the base current is

$$I_B = \frac{100,000}{\sqrt{3}(400)} = 144.3375 \text{ A}$$

The reactances on a common 100 MVA base are


$$X'_{dg1} = \frac{100}{60} (0.24) = 0.4\text{pu}$$

$$X'_{dg2} = \frac{100}{40} (0.24) = 0.6\text{pu}$$

$$X_t = \frac{100}{100} (0.16) = 0.16\text{pu}$$

$$X_{\text{line}} = \frac{160}{1600} = 0.1\text{pu}$$

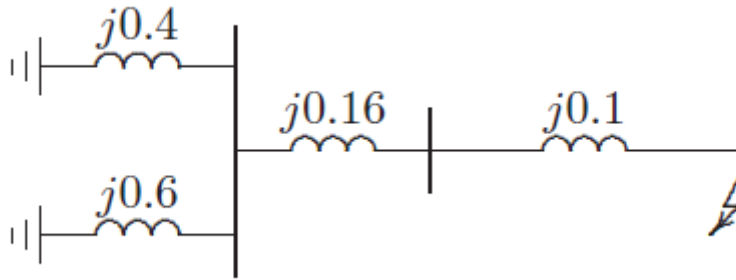The impedance diagram is as shown in figure below:.



Impedance to the point of fault is

$$X = j \frac{(0.4)(0.6)}{0.4 + 0.6} + j0.16 + j0.1 = j0.5\text{pu}$$

The fault current is

$$\begin{aligned} I_f &= \frac{1}{j0.5} = 2\angle -90^\circ \text{pu} \\ &= (144.3375)(2\angle -90^\circ) = 288.675\angle -90^\circ \text{ A} \end{aligned}$$

The Short-circuit MVA is

$$\text{SCMVA} = \sqrt{3}(400)(288.675)(10^{-3}) = 200\text{MVA}$$

SOLUTION QUESTION 2.


The impedance diagram is as shown in Figure 70.

(a) Impedance to the point of fault is

$$X = j \frac{(0.2)(0.3)}{0.2 + 0.3} = j0.12 \text{ pu}$$

The fault current is
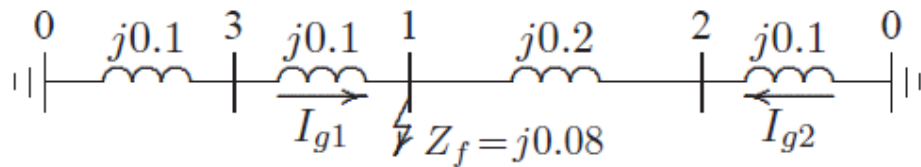
$$I_f = \frac{1}{j0.12 + j0.08} = 5 \angle -90^\circ \text{ pu}$$



(b)

$$\begin{aligned} V_1 &= (j0.08)(-j5) = 0.4 \text{ pu} \\ I_{g1} &= \frac{j0.3}{j0.5} (5) \angle -90^\circ = 3 \angle -90^\circ \text{ pu} \\ I_{g2} &= \frac{j0.2}{j0.5} (5) \angle -90^\circ = 2 \angle -90^\circ \text{ pu} \\ V_2 &= 0.4 + (j0.2)(-j2) = 0.8 \text{ pu} \\ V_3 &= 0.4 + (j0.1)(-j3) = 0.7 \text{ pu} \end{aligned}$$

SOLUTION QUESTION 3.

See lecture notes "ER66-W9-The Symmetrical Components (Fortescue Method)", from slide 47 to slide 50.

SOLUTION QUESTION 4. QUIZ

Q1 - Answer: C,D

Q2 - Answer: A,B,C,D

Q3 - Answer: C

Q4 - Answer: A

Q5 - Answer: C

Q6 - Answer: B

SOLUTION QUESTION 5

1 Subtransient Short-Circuit Current at Generator Terminals

Given data:

- $X_d'' = 0.15pu$
- Stator voltage = $20kV \times 1.05 = 21kV$
- Base impedance (not necessary):

$$Z_{base} = \frac{V_{base}^2}{S_{base}} = \frac{(20kV)^2}{500MVA} = 0.8\Omega$$

1 Subtransient short-circuit current (in kA):

$$I_{kA}'' = I_{pu}'' \times I_{base}$$

where:

$$I_{base} = \frac{S_{base}}{\sqrt{3} \cdot V_{base}}$$

2 Substituting values:

- $I_{pu}'' = 7pu$
- $I_{base} = \frac{500}{\sqrt{3} \cdot 20} = 14.43kA$

$$I_{kA}'' = 7 \times 14.43 = 101.01kA$$

3 Total Subtransient Short-Circuit Current

- Total reactance considering the subtransient time frame :

We do consider in this way the transformer, load and line impedance are in parallel with X_d'' as the fault occurs in the generator terminals.

$$X_{\text{total}} = X_d'' // X_m'' + X_L = 1/0.15 + 1/(0.20 + 0.305) = 0.1156 \text{ pu}$$

- Total short-circuit current (per unit):

$$I''_{\text{pu, total with load}} = \frac{1.05}{X_{\text{total}}} + \frac{1.05}{0.1156} = 9.079$$

- Total short-circuit current (kA):

$$I''_{\text{kA, total}} = I''_{\text{pu, total}} \times I_{\text{base}}$$

Substituting values:

$$I''_{\text{kA, total}} = 9.079 \times 14.43 = 131 \text{ kA}$$