
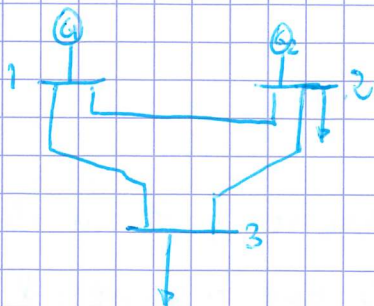


SOLUTION

Ex 1 -

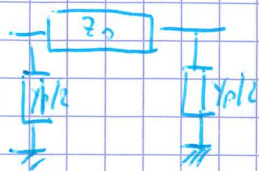

a) Each line is modelled as follows (T-model)



$$Y_0 = \frac{1}{Z_0}$$

Then

$$y_{11} = Y_0/2 + \frac{1}{Z_0} + Y_0/2 + \frac{1}{Z_0} = y_{22} = y_{33} = Y_0 + \frac{2}{Z_0}$$

off diagonal elements $y_{ij} = -\frac{1}{Z_0}$ ($i \neq j$)

Then Y_{bus} is

$$Y_{bus} = \begin{bmatrix} Y_0 + \frac{2}{Z_0} & -\frac{1}{Z_0} & -\frac{1}{Z_0} \\ -\frac{1}{Z_0} & Y_0 + \frac{2}{Z_0} & -\frac{1}{Z_0} \\ -\frac{1}{Z_0} & -\frac{1}{Z_0} & Y_0 + \frac{2}{Z_0} \end{bmatrix}$$

b) For bus 1 $S_1 = V_1 I_1^* = P_{G1} + jQ_{G1} = V_1 I_1^*$ (there is no load)
 $P_1 = P_{G1}$ $Q_1 = Q_{G1}$

For bus 2 $S_2 = (P_{G2} + jQ_{G2}) - (P_{L2} + jQ_{L2}) =$ (there is a generator and a load)
 $= (P_{G2} - P_{L2}) + j(Q_{G2} - Q_{L2})$

$$P_2 = P_{G2} - P_{L2} \quad Q_2 = Q_{G2} - Q_{L2}$$

For bus 3 $S_3 = V_3 I_3^* = (0 - P_{L3}) + j(0 - Q_{L3}) =$
 $= -P_{L3} - jQ_{L3}$

Thus

$$P_3 = -P_{L3}$$

$$Q_3 = -Q_{L3}$$

c)

- Since bus 2 is connected to a generator, it can be a PV bus (P_2 is given, $|V_2|$ is given, we have to compute Q_2 (Q_{G2}) and δ_2).
- Since bus 3 is connected to a load, it can be a PQ bus. P_3 and Q_3 are given, we have to compute $|V_3|$ and δ_3 .
- Bus 1 is a slack bus, so $|V_1|$ and δ_1 are known ($|V_1|=1$, for example, and $\delta_1=0$), and we have to compute P_1 and Q_1 .

d) For each bus i , ~~where~~ we have

~~$$I_i = \frac{S_i}{V_i^*}$$~~

$$I_1 = \frac{S_1^*}{V_1^*} = y_{11} V_1 + y_{12} V_2 + y_{13} V_3$$

$$I_2 = \frac{S_2^*}{V_2^*} = y_{21} V_1 + y_{22} V_2 + y_{23} V_3$$

$$I_3 = \frac{S_3^*}{V_3^*} = y_{31} V_1 + y_{32} V_2 + y_{33} V_3$$

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = Y_{bus} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

Then, in complex form, we have

$$S_1^* = y_{11} V_1 V_1^* + y_{12} V_1^* V_2 + y_{13} V_1^* V_3$$

$$S_2^* = y_{21} V_2^* V_1 + y_{22} V_2^* V_2 + y_{23} V_2^* V_3$$

$$S_3^* = y_{31} V_3^* V_1 + y_{32} V_3^* V_2 + y_{33} V_3^* V_3$$

Since $V_i = |V_i| e^{j\delta_i}$ and $y_{ij} = |y_{ij}| e^{j\delta_{ij}}$, we have

$$P_1 - jQ_1 = |y_{11}| e^{j\delta_{11}} |V_1|^2 + |y_{12}| e^{j\delta_{12}} |V_1| e^{-j\delta_1} |V_2| e^{j\delta_2} + |y_{13}| e^{j\delta_{13}} |V_1| e^{-j\delta_1} |V_3| e^{j\delta_3}$$

$$= |y_{11}| e^{j\delta_{11}} |V_1|^2 + |y_{12}| |V_1| |V_2| e^{j(\delta_2 - \delta_1 + \delta_{12})} + |y_{13}| |V_1| |V_3| e^{j(\delta_3 - \delta_1 + \delta_{13})}$$

Or

$$P_1 - jQ_1 = |y_{11}| |V_1| |V_1| e^{j(\delta_1 - \delta_1 + \delta_{11})} + |y_{12}| |V_1| |V_2| e^{j(\delta_2 - \delta_1 + \delta_{12})} + |y_{13}| |V_1| |V_3| e^{j(\delta_3 - \delta_1 + \delta_{13})}$$

Remembering that $e^{j\theta} = \cos\theta + j\sin\theta$, we can separate the real and the imaginary parts.

$$P_1 = |y_{11}| |V_1| |V_1| \cos(\delta_1 - \delta_1 + \delta_{11}) + |y_{12}| |V_1| |V_2| \cos(\delta_2 - \delta_1 + \delta_{12}) + |y_{13}| |V_1| |V_3| \cos(\delta_3 - \delta_1 + \delta_{13})$$

$$-Q_1 = |y_{11}| |V_1| |V_1| \sin(\delta_1 - \delta_1 + \delta_{11}) + |y_{12}| |V_1| |V_2| \sin(\delta_2 - \delta_1 + \delta_{12}) + |y_{13}| |V_1| |V_3| \sin(\delta_3 - \delta_1 + \delta_{13})$$

In compact form:

$$P_1 = \sum_{k=1}^3 |y_{1k}| |V_1| |V_k| \cos(\delta_k - \delta_1 + \delta_{1k})$$

$$-Q_1 = \sum_{k=1}^3 |y_{1k}| |V_1| |V_k| \sin(\delta_k - \delta_1 + \delta_{1k})$$

The same is for bus 2 and bus 3

$$P_2 = \sum_{k=1}^3 |y_{2k}| |V_2| |V_k| \cos(\delta_k - \delta_2 + \delta_{2k})$$

$$-Q_2 = \sum_{k=1}^3 |y_{2k}| |V_2| |V_k| \sin(\delta_k - \delta_2 + \delta_{2k})$$

$$P_3 = \sum_{k=1}^3 |y_{3k}| |V_3| |V_k| \cos(\delta_k - \delta_3 + \delta_{3k})$$


$$-Q_3 = \sum_{k=1}^3 |y_{3k}| |V_3| |V_k| \sin(\delta_k - \delta_3 + \delta_{3k})$$

Or in general

$$\left. \begin{aligned} P_i &= \sum_{k=1}^3 |y_{ik}| |V_i| |V_k| \cos(\delta_k - \delta_i + \delta_{ik}) \\ -Q_i &= \sum_{k=1}^3 |y_{ik}| |V_i| |V_k| \sin(\delta_k - \delta_i + \delta_{ik}) \end{aligned} \right\}$$

$i = 1, 2, 3$

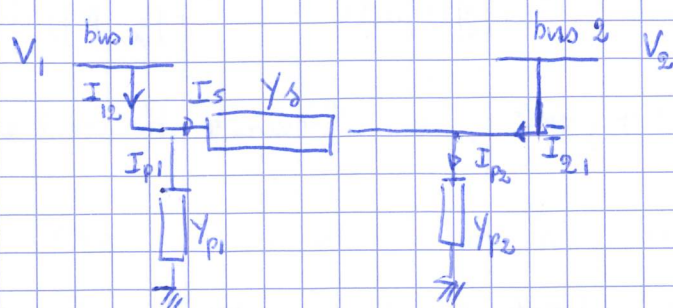
e) Once all voltages are known for all buses, the power flows on the various lines of the network are computed by using the π -model of the line.



Then $I_{12} = I_s + I_{p1} = (V_1 - V_2)Y_d + V_1Y_{p1}$ $I_{21} = -I_s + I_{p2} = (V_2 - V_1)Y_d + V_2Y_{p2}$

Thus $S_{12} = P_{12} + jQ_{12} = V_1 I_{12}^* = V_1 (V_1^* - V_2^*)Y_d^* + |V_1|^2 Y_{p1}^*$
 $S_{21} = P_{21} + jQ_{21} = V_2 I_{21}^* = V_2 (V_2^* - V_1^*)Y_d^* + |V_2|^2 Y_{p2}^*$

- Ex 2 -

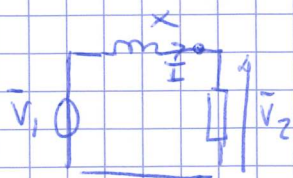

$$S_2 = V_2 I^*$$

but $I = \frac{V_1 - V_2}{jX}$ so $S_2 = \frac{V_2 (V_2 - V_1)^*}{-jX} =$

then

$$S_2 = \frac{j V_2 V_1^* - |V_2|^2}{X}$$

$$\left(\frac{1}{j} = -j\right)$$

We impose $V_1 = |V_1| e^{j0}$ and $V_2 = |V_2| e^{-j\delta_2}$

That is we consider V_1 to be the reference voltage

so



~~... and the power flow is ...~~

Under these assumptions we have

$$S_2 = j \frac{|V_2| e^{j\delta_2} |V_1| - |V_2|^2}{X}$$

Since $e^{j\delta_2} = \cos \delta_2 + j \sin \delta_2$, we have:

$$S_2 = \frac{j(|V_1||V_2| \cos \delta_2 + j|V_1||V_2| \sin \delta_2) - j|V_2|^2}{X} =$$

$$= \frac{(|V_1||V_2| \sin \delta_2)}{X} + j \frac{|V_1||V_2| \cos \delta_2 - |V_2|^2}{X}$$

Thus $\begin{cases} P = \frac{|V_1||V_2| \sin \delta}{X} \\ Q = \frac{|V_1||V_2| \cos \delta - |V_2|^2}{X} \end{cases} \quad \delta = \delta_2$

$\delta = \delta_2$ is the angle between phasor $\bar{V}_1$ and $\bar{V}_2$; it is considered positive ~~when $\bar{V}_1$ lags $\bar{V}_2$~~ when $\bar{V}_1$ leads $\bar{V}_2$, so that $P > 0$.

Question 3

$$C_1 = 10P_1 + 0.008P_1^2 \quad \$/h$$

$$C_2 = 8P_2 + 0.009P_2^2 \quad \$/h$$

$$P_T = 1500 \text{ MW}$$

1. Since there are no transmission losses, the optimal economical dispatch is obtained when $IC_1 = IC_2$,

$$IC_1 = \frac{dC_1}{dP_1} = 10 + 0.016P_1 \quad \$/MWh$$

$$IC_2 = \frac{dC_2}{dP_2} = 8 + 0.018P_2 \quad \$/MWh$$

Remembering that $P_2 = P_T - P_1$, and that $IC_1 = IC_2$, we have

$$10 + 0.016P_1 = 8 + 0.018(P_T - P_1)$$

$$0.016P_1 = 0.018(1500 - P_1) - 2$$

$$0.016P_1 = 27 - 0.018P_1 - 2 = 25 - 0.018P_1$$

$$0.034P_1 = 25 \quad P_1 = 735.28 \text{ MW}$$

$$P_2 = 1500 - P_1 = 764.72$$

2. $IC_1 = IC_2 = 10 + 0.016P_1 = 21.76 \quad \$/MWh$

3. $C_T = C_1 + C_2 = 10 \cdot 735.28 + 0.008(735.28)^2 + 8 \cdot 764.72 + 0.009(764.72)^2 = 23,058 \quad \$/h$

- Question 4 -

$$a) \quad G(s) = \frac{k_a k_e k_f}{(1+T_a s)(1+T_e s)(1+T_f s)}$$

Type 0, ~~since~~ since there are no poles in the origin

b) The closed loop of the system, defining $K = k_a k_e k_f$, is

$$W(s) = \frac{K}{(1+T_a s)(1+T_e s)(1+T_f s) + K}$$

Then

$$\Delta y = W(s) \Delta u(s)$$

If $u(s)$ is a step input, then $u(s) = \frac{1}{s}$. The output would be therefore:

$$\Delta y(s) = W(s) \frac{1}{s}$$

In steady state $\Delta y(\infty) = \lim_{s \rightarrow 0} s \Delta y(s)$ (Final value theorem),

so, calling Δy_{ss} the value at steady state $\Delta y(\infty)$

$$\Delta y_{ss} = \lim_{s \rightarrow 0} \left[s W(s) \frac{1}{s} \right] = W(0)$$

$$W(0) = \frac{K}{1+K}$$

The error between the input value 1 and the steady-state response is

$$\Delta e_{ss} = 1 - \frac{K}{1+K} = \frac{1}{1+K}$$

~~Since $\Delta e_{ss} \leq 0.01$, we have $K \geq 99$~~

But Δe_{ss} is requested to be less than 1%, or 0.01, so:

$$\frac{1}{1+K} \leq 0.01 \quad \text{or} \quad K \geq 99$$

$$G(s) = \frac{K_a}{(s+0.1)(s+0.4)(s+1)} \quad p_1 = -1 \quad p_2 = -2.5 \quad p_3 = -10$$

$$= \frac{K_a}{(0.1)(0.4)(s+1)(s+2.5)(s+10)} = \frac{25 K_a}{(s+1)(s+10)(s+2.5)}$$

$$q = n - m = 3$$

$$\gamma = 60^\circ, 0^\circ, -60^\circ$$

$$\sigma_a = \frac{\sum p_i - \sum z_i}{3} = \frac{-13.5}{3} = -4.5$$

$$P(s) = (s+1)(s+10)(s+2.5) + 25 K_a = s^3 + 13.5s^2 + 37.5s + 25(1+K_a)$$

s^3	1	37.5
s^2	13.5	$25(1+K_a)$
s^1	$37.5 - 0.66(1+K_a)$	
s^0	$25(1+K_a)$	

$$s^1 = \frac{13.5 \cdot 37.5 - 25(1+K_a)}{37.5} = \frac{13.5}{37.5} - 0.66(1+K_a)$$

We must have

$$1+K_a > 0 \quad K_a > -1 \rightarrow K_a > 0$$

$$\frac{13.5}{37.5} - 0.66 - 0.66 K_a > 0$$

$$\frac{12.83}{37.5} - 0.66 K_a > 0 \quad K_a < \frac{12.83}{37.5 \cdot 0.66} = 19.44$$

$$\text{Thus } 0 \leq K_a \leq 19.44$$


$$25(1+K_a) \approx 511$$

Auxiliary equation: 511

$$13.5s^2 + 37.8 = 0$$

$$s^2 + 37.8 = 0$$
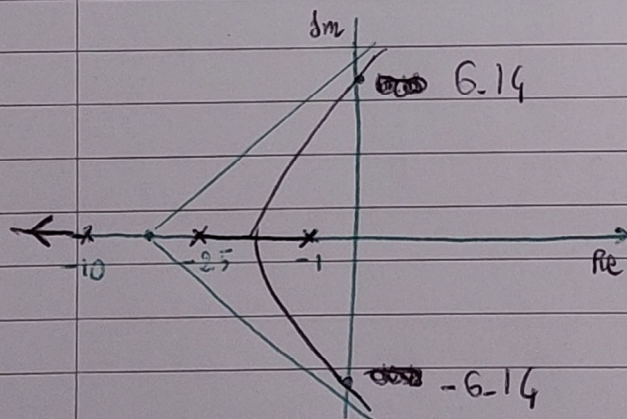
$$s = \pm j \sqrt{\frac{37.8}{13.5}} = \pm j 6.14$$



$$\sigma_a = -4.5$$