

ER66 MIDTERM EXAM

5 novembre 2024 de 10h15 à 12h15 en salle A201 et A202 à Belfort


*The use of lecture notes is not allowed.
You can reply either in English or in French.
Use of programmable calculators is not allowed.*

The exam consists of two sections: A and B. Section A contains only one question worth 10 marks, which you must answer. Section B contains three questions, each worth 5 marks, and you are required to answer two of them. The maximum score is 20 marks.

Section A: COMPULSORY QUESTION

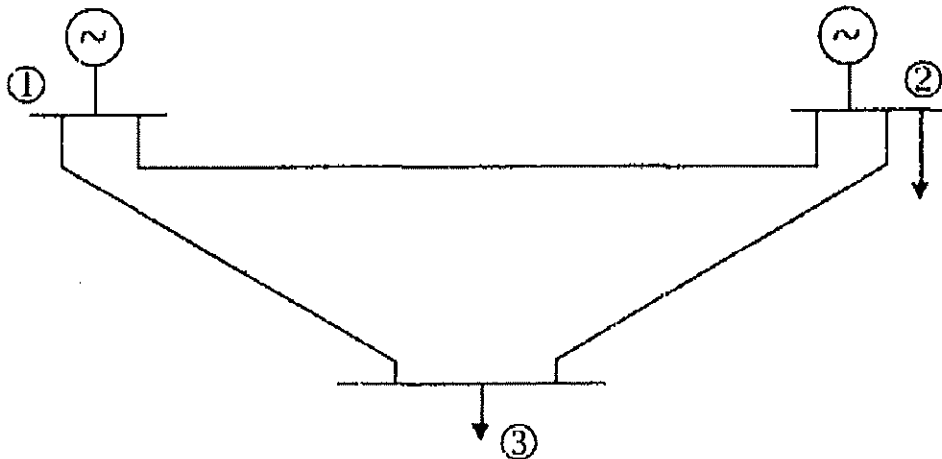QUESTION A1 (10 MARKS)

For the simple three bus system below, write the load flow equations.



Choose Bus 1 as the reference bus, and, for simplicity, assume that the lines have all the same series impedance Z_s and the admittance $Y_p/2$ in the π - model of the line.

- (a) Construct the admittance matrix. (2 mark)
- (b) For each bus, define the net complex power, noting that Bus 2 is connected to both a generator and a load, while Bus 3 is connected only to a load. (1 mark)


- (c) Determine which buses can be PV or PQ and justify your choice. Specify also the known and unknown variables for each bus. (1 mark)
- (d) Prove, in general, that the load flow equations in real form for each bus are given by:

$$P_i = \sum_{k=1}^3 |y_{ik}| |V_i| |V_k| \cos(\delta_k - \delta_i + \gamma_{ik})$$

$$Q_i = - \sum_{k=1}^3 |y_{ik}| |V_i| |V_k| \sin(\delta_k - \delta_i + \gamma_{ik}) \text{ for } i = 1, 2, 3$$

Remark: Consider each element of the admittance matrix in the polar form: $y_{ij} = |y_{ij}| e^{j\gamma_{ij}}$ (4 mark).

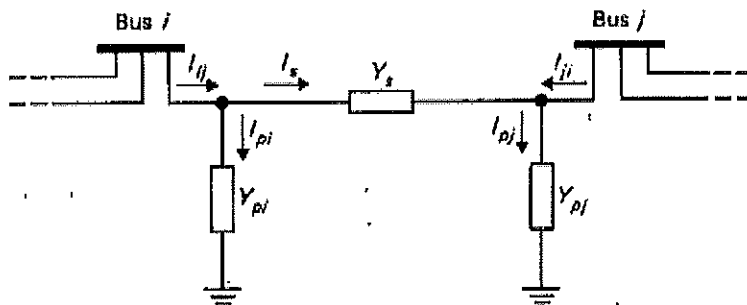- (e) Assuming the equations above are solved, yielding the voltage magnitudes and phases at each node, explain how to calculate the power flows between bus 1 and bus 2 and viceversa. Use the figure below, taken from the course slides.




(2 mark)

Section B: solve 2 out of the following 3 exercises

QUESTION B1 (5 MARKS)

Consider the following figure:

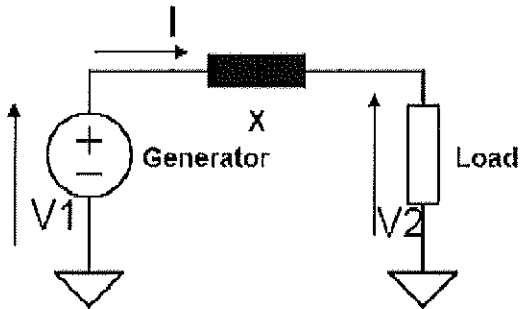

This figure shows a generator connected to a load through a reactance, which includes both the generator and line reactances. The real power transmitted by the generator and the reactive power supplied to the load, assuming a constant voltage V_2 , are given by the following formulas:

$$P = \frac{|V_1||V_2|}{X} \sin \delta \quad \text{MW/phase}$$
$$Q_2 = \frac{|V_1||V_2| \cos \delta - |V_2|^2}{X} \quad \text{Mvar/phase}$$

- a) Prove the first formula (2 marks)
- b) Prove the second formula (2 marks)
- c) When is the real flow positive, that is when does it enter the load? In other words when is δ positive and how is it defined? (1 mark)

QUESTION B2 (5 MARKS)

An area of an interconnected power system has two fossil-fuel units operating under economic dispatch. The variable operating costs of these units are given by:

$$C_1 = 10P_1 + 8 \times 10^{-3}P_1^2 \text{ \$/h}$$
$$C_2 = 8P_2 + 9 \times 10^{-3}P_2^2 \text{ \$/h}$$

where P_1 and P_2 are in megawatts.

Determine, when the total load demand P_T is 1500 MW,

1. The power output of each unit under economic dispatch. (3 marks)
2. The incremental operating cost. (1 mark)
3. The total operating cost C_T that minimizes C_T (1 mark)

Assume that generating unit inequality constraints and transmission losses are neglected.

QUESTION B3 (5 MARKS)

The block-diagram representation of a closed-loop automatic regulating system, in which generator voltage control is accomplished by controlling the exciter voltage, is shown in the figure below. T_a , T_e , and T_f are the time constants associated with the amplifier, exciter, and generator field circuit, respectively.

- (a) Find the open-loop transfer function $G(s)$ and deduce the type of the system, by giving proper explanation. (1 mark)
- (b) Evaluate the minimum open-loop gain such that, for a unit step input, the steady-state error Δe_{ss} does not exceed 1%. (2 marks)
- (c) Draw a qualitative root locus of the system as the amplifier gain k_a varies and determine its stability limit. Given parameters are $T_f = 1$, $T_e = 0.4$, $T_a = 0.1$, and $k_e = k_f = 1$.

Calculate only the real root locus, the angles of the asymptotes, their intercept on the real axis, and the intercept on the imaginary axis using the Routh-Hurwitz Criterion. (2 marks)

